

**Grade 6 Understanding Matter and Energy – Electricity and Electrical Devices** 

## **A GRAPHITE CIRCUIT**

Fill the empty spaces using a pencil. Then tape the LED light bulb in place and position the battery as shown.



